

The industry's most advanced
90nm ARM9 microcontroller

PHILIPS
sense and sin


[Design Briefs]

Divide And Conquer The Resistive Divider

Karl R. Volk
ED Online ID #12236
April 13, 2006

Copyright © 2006 Penton Media, Inc., All rights reserved.

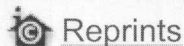Printing of this document is for personal use only.



The resistive voltage divider—a basic circuit taught in every introductory electronics course—may cause some problems during its implementation. If you've ever stood in front of a resistor kit while punching values into your calculator, this article is for you.

Typical kits don't include every value. So, finding an elusive ratio for which both values are commonly available can be a challenge. The small spreadsheet described below not only provides a table of 1% resistor values, it also makes it a snap to find the ratio you need using two available resistors.

Most engineers don't know that 1% resistor values are logarithmically spaced in increments of exactly 1/96th of a decade. Figure 1 shows a spreadsheet table of 1% resistor values, rounded to three significant digits. For example, the formula in cell B5 is $=10^{((B\$4+\$A5)/96)}$, which is copied to B5 through G20. Only the yellow highlighted values are commonly available in resistor kits. A typical kit contains slightly more than one-fourth of the values.

In a typical application for resistive dividers, the divider ratio $R2/(R1 + R2)$ supplies external feedback to the 4-MHz regulated stepdown converter (Fig. 2). (The feedback threshold at the FB terminal is 0.6 V, and the desired output is 1.5 V.)

To calculate values for R1 and R2, enter the regulator's desired output voltage (voltage at the top of the divider) in cell B3 and the regulator's feedback threshold (voltage at the divider midpoint) in cell C3. Then, the spreadsheet formula in cell D3 is $=96*\text{LOG}(B3/C3-1)$, which returns a value of +16.9 steps for this example. That result is the number of 1% resistor-value steps separating R1 from R2.

Therefore, if you use $R2 = 100 \text{ k}\Omega$ (cell B5), you would move +17 steps down the list to $R1 = 150 \text{ k}\Omega$ (cell C6). That would be a good choice because both

resistors are highlighted in yellow (commonly available). Very quickly from the spreadsheet table, you can see that $R2 = 110\text{ k}\Omega$ isn't a good choice for this example because $R1 = 165\text{ k}\Omega$ isn't commonly available. You can also quickly identify an exhaustive list of commonly available resistor values that would be suitable: 1.00:1.50, 1.21:1.82, 1.62:2.43, 1.82:2.74, 2.00:3.01, 2.21:3.32, 3.32:4.99, and 4.99:7.50. When the number of steps (D3) is negative, R1 is less than R2. Therefore, you should move in the opposite direction on the value list. In either direction, you may wrap around the list from 9.76 to 1.00, which means that you've moved to the next decade of resistance values. If you use resistive dividers for purposes other than regulator feedback, you may wish to rename cells B2 and C2 as "Vtop" and "Vmid," respectively.


The [Figure 1](#) spreadsheet is available for download in Microsoft Excel format (DB2195XLspreadsheet.xls) and also in Pocket Excel format for Pocket PC (DB2195POCKETXLspreadsheet.PXL), formatted to fit the Pocket PC screen at 60% zoom, at ED Online 12236 at www.electronicdesign.com.

FOLDER.GIF



Figure 1

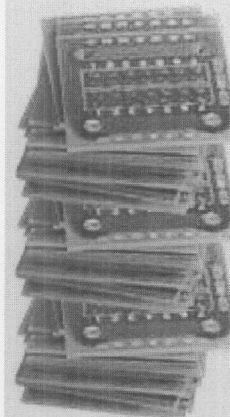Best PCB
online
service
from
Quote to
Delivery



www.sunstone.com


CLICK HERE

SUNSTONE

	A	B	C	D	E	F	G
1	1% Standard Resistor-Dividers						
2		Vout	Vfb	Steps			
3		1.5	0.6	16.9			
4		0	16	32	48	64	80
5	0	1.00	1.47	2.15	3.16	4.64	6.81
6	1	1.02	1.50	2.21	3.24	4.75	6.98
7	2	1.05	1.54	2.26	3.32	4.87	7.15
8	3	1.07	1.58	2.32	3.40	4.99	7.32
9	4	1.10	1.62	2.37	3.48	5.11	7.50
10	5	1.13	1.65	2.43	3.57	5.23	7.68
11	6	1.15	1.69	2.49	3.65	5.36	7.87
12	7	1.18	1.74	2.55	3.74	5.49	8.06
13	8	1.21	1.78	2.61	3.83	5.62	8.25
14	9	1.24	1.82	2.67	3.92	5.76	8.45
15	10	1.27	1.87	2.74	4.02	5.90	8.66
16	11	1.30	1.91	2.80	4.12	6.04	8.87
17	12	1.33	1.96	2.87	4.22	6.19	9.09
18	13	1.37	2.00	2.94	4.32	6.34	9.31
19	14	1.40	2.05	3.01	4.42	6.49	9.53
20	15	1.43	2.10	3.09	4.53	6.65	9.76

1. This spreadsheet not only lists 1% resistor values, it also lets you find the divider needed using two commonly available resistors.

Figure 2

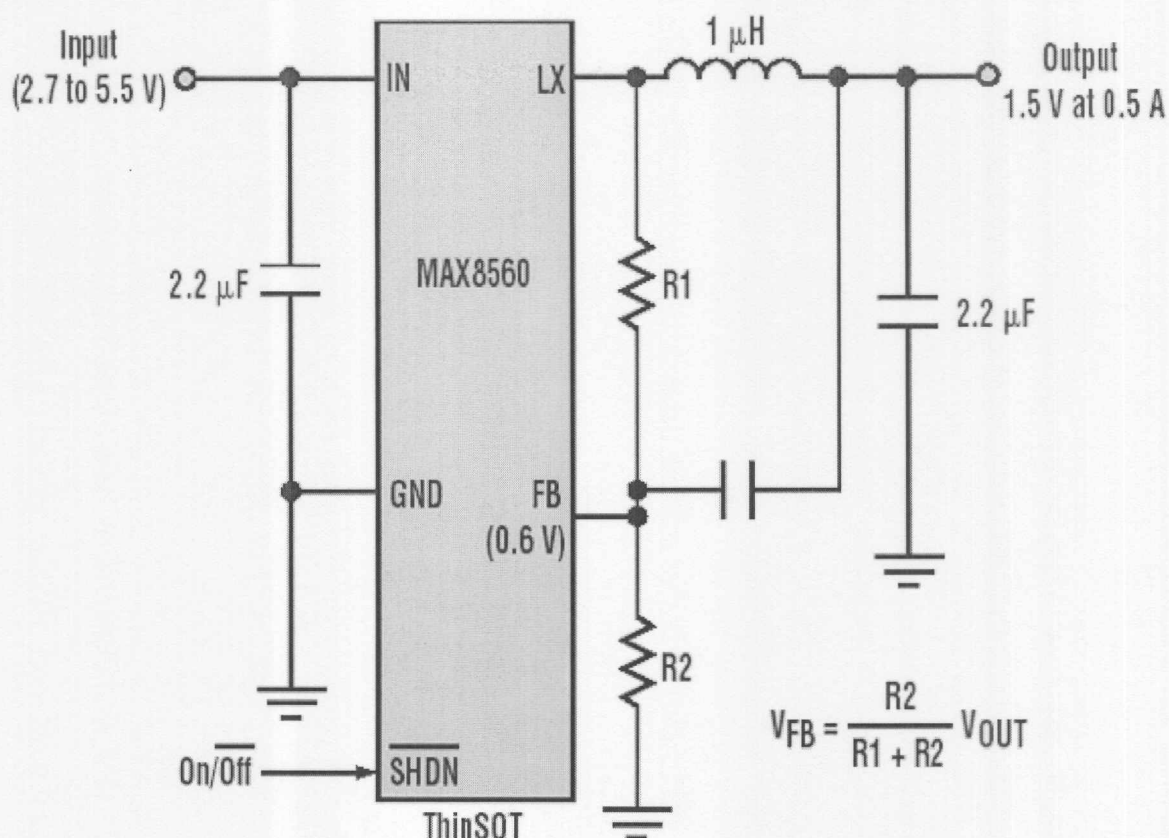

2. The divider ratio $R2/(R1 + R2)$ sets the output voltage for this 4-MHz stepdown regulator. With Figure 1's spreadsheet, you can select R1 and R2 from commonly available values.

HTMLFILE.GIF



Resources



Electronic Design Europe



EEPN



Microwaves & RF



Wireless Systems Design



Discover Circuits



Find Power Products



Military Electronics



Featured Vendors



Electronic Design E-Cards



Free Design Resources



Job Board



Ideas for Design



Basics of Design



Design FAQs



Events

Part Finder

brought to you by:



RSS Feeds

- Electronic Design
- Microwaves & RF
- EE Product News

Marketplace

The Cadence RF Design Methodology Kit

Intelligently manage parasitic extraction. Link system-level design with IC implementation. Accurately and rapidly verify complete wireles

Learn more>>>

Looking for a Reliable Standard Linear Supplier?

Texas Instruments offers a broad portfolio of Standard Linear products that includes analog switches, op amps, standard interface, and management products. For more information or to order free samples visit TI's new Standard Linear Webpage.

Feel like the microcontrollers you're using are limiting?

Need more performance and flexibility for your next application? Our AVR microcontrollers are here to help! Click here to receive the AVR guide.

Free Agilent CD-ROM

Free Agilent CD-ROM: Video demo, literature for Signal Source Analyzer and more.

Electronic Design Ebooks from National Semiconductor, Arrow, Keithley and more!

Download a free Ebook from our library and stay up-to-date on current trends and technologies. Technical resources are compiled by Electronic Design and available for immediate download to your PC.

Sponsored Links

Embedded System Design

Eng. Development H/W & S/W. View Specs, Request Quote & Shop Online.

www.arrowdevtools.com

PSS

Proven Software Solutions Pioneers in embedded software reuse

www.proven-software.com

Custom Electronic Designs


Control Electronics and Programming Quick Designs & prototypes

www.gunnsys.com

Intel? Embedded Solutions

Meet development challenges & speed time to market w/ Intel in embedded

intel.com

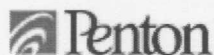

[Planet EE Network Home](#) | [Contact Us](#) | [Editorial Calendar](#) | [Media Kit](#) | [Headlines](#) | [Site Feedback & Bugs](#)
Copyright © 2006 Penton Media, Inc., All rights reserved. [Legal](#) | [Privacy](#)